


GLOBAL
EDITION



Electric Circuits

TENTH EDITION

James W. Nilsson • Susan A. Riedel

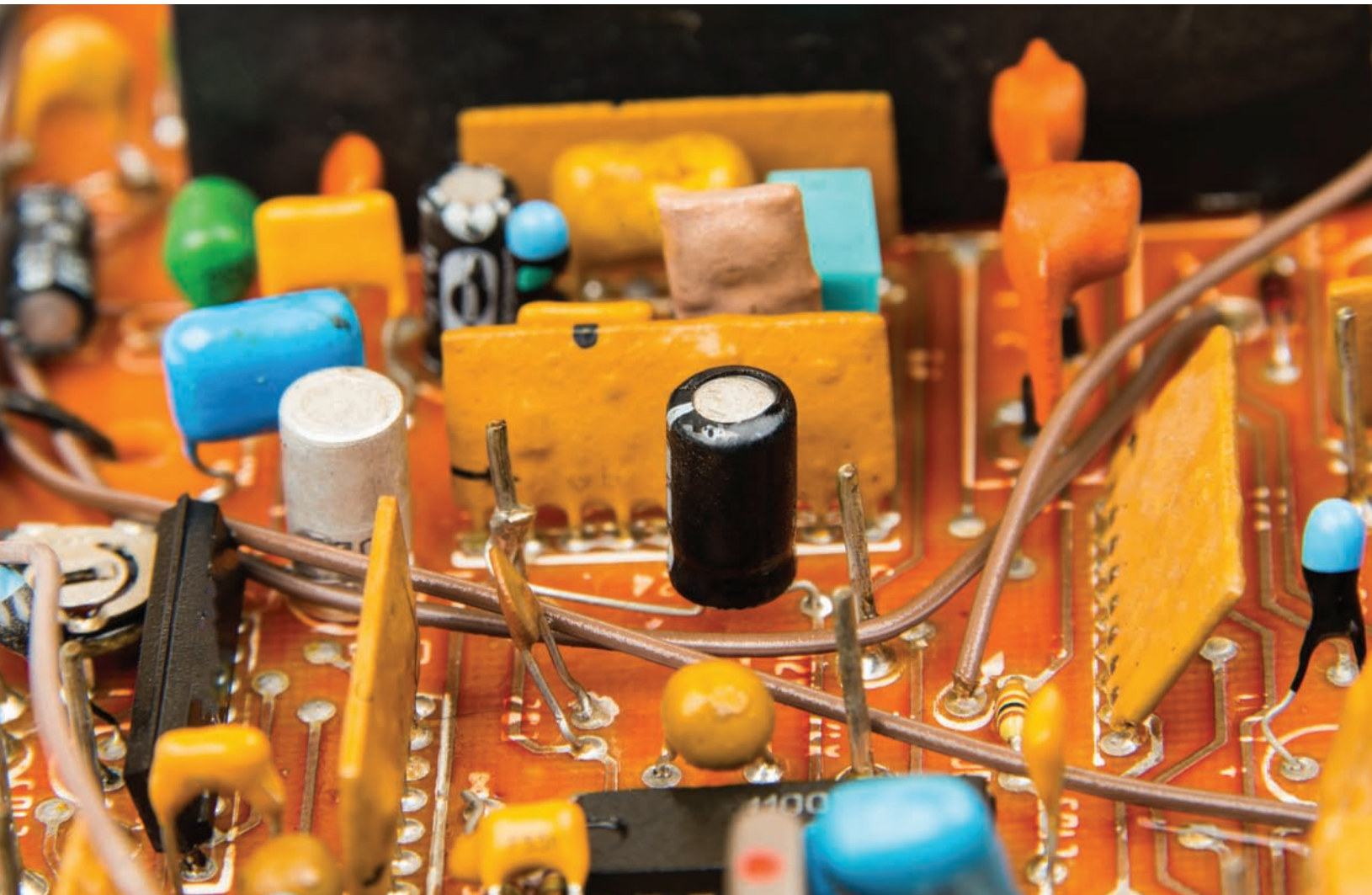

ALWAYS LEARNING

PEARSON

ELECTRIC CIRCUITS

TENTH EDITION

GLOBAL EDITION

This page is intentionally left blank.

ELECTRIC CIRCUITS

TENTH EDITION
GLOBAL EDITION

James W. Nilsson

*Professor Emeritus
Iowa State University*

Susan A. Riedel

Marquette University

PEARSON

Boston Columbus Indianapolis New York San Francisco Upper Saddle River
Amsterdam Cape Town Dubai London Madrid Milan Munich Paris Montréal Toronto
Delhi Mexico City São Paulo Sydney Hong Kong Seoul Singapore Taipei Tokyo

Vice President and Editorial Director: Marcia J. Horton
Acquisitions Editor: Andrew Gilfillan
Editorial Assistant: William Opaluch
Marketing Manager, Global Edition: Bram Van Kempen
Senior Managing Editor: Scott Disanno
Production Editor: Rose Kernan
Head, Learning Asset Acquisition,
Global Edition: Laura Dent
Acquisitions Editor, Global Edition: Karthik
Subramaniun
Project Editor, Global Edition: Aaditya Bugga

Cover Photograph: oksana2010 / Shutterstock
Senior Manufacturing Controller, Global Edition:
Trudy Kimber
Media Producer, Global Edition: Anuprova Dey
Chowdhuri
Senior Operations Supervisor: Alan Fischer
Design Manager: Kenny Beck
Manager, Rights and Permissions: Zina Arabia
Full-Service Project Management: Integra Publishing
Services
Cover Printer: Courier Kendallville

Pearson Education Limited
Edinburgh Gate
Harlow
Essex CM20 2JE
England

and Associated Companies throughout the world

Visit us on the World Wide Web at:
www.pearsonglobaleditions.com

© Pearson Education Limited, 2015

The rights of James W. Nilsson and Susan A. Riedel to be identified as the authors of this work have been asserted by them in accordance with the Copyright, Designs and Patents Act 1988.

Authorized adaptation from the United States edition, entitled Electric Circuits, 10th edition, ISBN 978-0-13-376003-3, by James W. Nilsson and Susan A. Riedel, published by Pearson Education © 2015.

All rights reserved. No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means, electronic, mechanical, photocopying, recording or otherwise, without either the prior written permission of the publisher or a license permitting restricted copying in the United Kingdom issued by the Copyright Licensing Agency Ltd, Saffron House, 6–10 Kirby Street, London EC1N 8TS.

All trademarks used herein are the property of their respective owners. The use of any trademark in this text does not vest in the author or publisher any trademark ownership rights in such trademarks, nor does the use of such trademarks imply any affiliation with or endorsement of this book by such owners.

ISBN 10: 1-292-06054-9
ISBN 13: 978-1-292-06054-5 (Print)
ISBN 13: 978-1-292-06547-2 (PDF)

British Library Cataloguing-in-Publication Data

A catalogue record for this book is available from the British Library

10 9 8 7 6 5 4 3 2 1
14 13 12 11 10

Typeset in 10/12 TimesTen-Roman by Integra Publishing Services.
Printed and bound by Courier Kendallville in the United States of America.

To Anna

This page is intentionally left blank.



Brief Contents

	List of Examples	13
	Preface	17
Chapter 1	Circuit Variables	24
Chapter 2	Circuit Elements	46
Chapter 3	Simple Resistive Circuits	78
Chapter 4	Techniques of Circuit Analysis	110
Chapter 5	The Operational Amplifier	166
Chapter 6	Inductance, Capacitance, and Mutual Inductance	196
Chapter 7	Response of First-Order RL and RC Circuits	234
Chapter 8	Natural and Step Responses of RLC Circuits	286
Chapter 9	Sinusoidal Steady-State Analysis	326
Chapter 10	Sinusoidal Steady-State Power Calculations	380
Chapter 11	Balanced Three-Phase Circuits	418
Chapter 12	Introduction to the Laplace Transform	448
Chapter 13	The Laplace Transform in Circuit Analysis	486
Chapter 14	Introduction to Frequency Selective Circuits	542
Chapter 15	Active Filter Circuits	578
Chapter 16	Fourier Series	624
Chapter 17	The Fourier Transform	664
Chapter 18	Two-Port Circuits	698
Appendix A	The Solution of Linear Simultaneous Equations	725
Appendix B	Complex Numbers	745
Appendix C	More on Magnetically Coupled Coils and Ideal Transformers	751
Appendix D	The Decibel	759
Appendix E	Bode Diagrams	761
Appendix F	An Abbreviated Table of Trigonometric Identities	779
Appendix G	An Abbreviated Table of Integrals	781
Appendix H	Common Standard Component Values	783
	Answers to Selected Problems	785
	Index	797

This page is intentionally left blank.

Contents

List of Examples 13

Preface 17

Chapter 1 Circuit Variables 24

Practical Perspective: Balancing Power 25

1.1 Electrical Engineering: An Overview 26

1.2 The International System of Units 30

1.3 Circuit Analysis: An Overview 32

1.4 Voltage and Current 33

1.5 The Ideal Basic Circuit Element 34

1.6 Power and Energy 36

Practical Perspective: Balancing Power 39

Summary 40

Problems 41

Chapter 2 Circuit Elements 46

Practical Perspective: Heating with Electric Radiators 47

2.1 Voltage and Current Sources 48

2.2 Electrical Resistance (Ohm's Law) 52

2.3 Construction of a Circuit Model 56

2.4 Kirchhoff's Laws 59

2.5 Analysis of a Circuit Containing Dependent Sources 64

Practical Perspective: Heating with Electric Radiators 68

Summary 70

Problems 70

Chapter 3 Simple Resistive Circuits 78

Practical Perspective: Resistive Touch Screens 79

3.1 Resistors in Series 80

3.2 Resistors in Parallel 81

3.3 The Voltage-Divider and Current-Divider Circuits 83

3.4 Voltage Division and Current Division 86

3.5 Measuring Voltage and Current 88

3.6 Measuring Resistance—The Wheatstone Bridge 91

3.7 Delta-to-Wye (Pi-to-Tee) Equivalent Circuits 93

Practical Perspective: Resistive Touch Screens 95

Summary 97

Problems 98

Chapter 4 Techniques of Circuit Analysis 110

Practical Perspective: Circuits with Realistic Resistors 111

4.1 Terminology 112

4.2 Introduction to the Node-Voltage Method 115

4.3 The Node-Voltage Method and Dependent Sources 117

4.4 The Node-Voltage Method: Some Special Cases 118

4.5 Introduction to the Mesh-Current Method 121

4.6 The Mesh-Current Method and Dependent Sources 124

4.7 The Mesh-Current Method: Some Special Cases 125

4.8 The Node-Voltage Method Versus the Mesh-Current Method 128

4.9 Source Transformations 131

4.10 Thévenin and Norton Equivalents 135

4.11 More on Deriving a Thévenin Equivalent 139

4.12 Maximum Power Transfer 142

4.13 Superposition 144

Practical Perspective: Circuits with Realistic Resistors 147

Summary 151

Problems 152

Chapter 5 The Operational Amplifier 166

Practical Perspective: Strain Gages 167

5.1 Operational Amplifier Terminals 168

5.2 Terminal Voltages and Currents 168

5.3 The Inverting-Amplifier Circuit 172

5.4 The Summing-Amplifier Circuit 174

5.5 The Noninverting-Amplifier Circuit 175

5.6 The Difference-Amplifier Circuit 177

5.7 A More Realistic Model for the Operational Amplifier 181

Practical Perspective: Strain Gages 184

Summary 186

Problems 187