
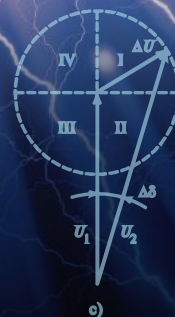


CRC CRC Press
Taylor & Francis Group

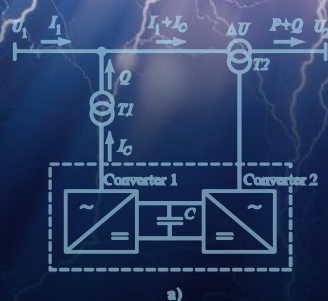

Power Electronics Basics

OPERATING PRINCIPLES, DESIGN, FORMULAS, AND APPLICATIONS



Yuriy Rozanov • Sergey Ryvkin
Evgeny Chaplygin • Pavel Voronin

Power Electronics Basics

OPERATING PRINCIPLES, DESIGN,
FORMULAS, AND APPLICATIONS

Power Electronics Basics

OPERATING PRINCIPLES, DESIGN,
FORMULAS, AND APPLICATIONS

Yuriy Rozanov • Sergey Ryvkin
Evgeny Chaplygin • Pavel Voronin



CRC Press

Taylor & Francis Group

Boca Raton London New York

CRC Press is an imprint of the
Taylor & Francis Group, an **informa** business

CRC Press
Taylor & Francis Group
6000 Broken Sound Parkway NW, Suite 300
Boca Raton, FL 33487-2742

© 2016 by Taylor & Francis Group, LLC
CRC Press is an imprint of Taylor & Francis Group, an Informa business

No claim to original U.S. Government works
Version Date: 20150305

International Standard Book Number-13: 978-1-4822-9880-2 (eBook - PDF)

This book contains information obtained from authentic and highly regarded sources. Reasonable efforts have been made to publish reliable data and information, but the author and publisher cannot assume responsibility for the validity of all materials or the consequences of their use. The authors and publishers have attempted to trace the copyright holders of all material reproduced in this publication and apologize to copyright holders if permission to publish in this form has not been obtained. If any copyright material has not been acknowledged please write and let us know so we may rectify in any future reprint.

Except as permitted under U.S. Copyright Law, no part of this book may be reprinted, reproduced, transmitted, or utilized in any form by any electronic, mechanical, or other means, now known or hereafter invented, including photocopying, microfilming, and recording, or in any information storage or retrieval system, without written permission from the publishers.

For permission to photocopy or use material electronically from this work, please access www.copyright.com (<http://www.copyright.com/>) or contact the Copyright Clearance Center, Inc. (CCC), 222 Rosewood Drive, Danvers, MA 01923, 978-750-8400. CCC is a not-for-profit organization that provides licenses and registration for a variety of users. For organizations that have been granted a photocopy license by the CCC, a separate system of payment has been arranged.

Trademark Notice: Product or corporate names may be trademarks or registered trademarks, and are used only for identification and explanation without intent to infringe.

Visit the Taylor & Francis Web site at
<http://www.taylorandfrancis.com>

and the CRC Press Web site at
<http://www.crcpress.com>

Contents

Preface.....	xiii
Authors	xv

Chapter 1 Basic concepts and terms in power electronics.....	1
1.1 Conversion of electrical energy: Classification of converters.....	1
1.2 Output parameters and characteristics of converters	4
1.3 Influence of converters on the grid	8
1.4 Basic converter parameters	12
1.5 ac and dc filters	14
1.5.1 Dynamic processes in filters	18
References	19

Chapter 2 Semiconductor power switches and passive components.....	21
2.1 Introduction.....	21
2.2 Power diodes	21
2.2.1 Power diodes with $p^+n^-n^+$ structure	21
2.2.2 Schottky power diodes	24
2.2.3 Pulsed diodes	25
2.3 Power bipolar transistors.....	27
2.4 Thyristors.....	32
2.4.1 Controllable semiconductor switches with $p-n-p-n$ structure.....	32
2.4.2 Power photothyristors.....	37
2.4.3 Symmetric thyristors.....	39
2.5 Switched thyristors.....	41
2.5.1 The GTO thyristor	41
2.5.2 Gate-commutated thyristors (GCTs, ETOs, MTOs)	43
2.5.3 The integrated GCT thyristor	46
2.5.4 The MOS-controlled thyristor	46
2.6 Field transistors.....	47
2.6.1 Powerful short-channel MOS transistors.....	47

2.6.2	CoolMOS technology	53
2.6.3	Static induction transistors.....	55
2.7	The IGBT	58
2.7.1	Epitaxial (PT) and homogeneous (NPT) IGBT structures.....	64
2.7.2	Trench-gate IGBT	65
2.7.3	The trench-FS and SPT.....	67
2.7.4	The CSTBT and SPT+	68
2.8	Switch modules.....	69
2.8.1	Topology of integrated power modules	69
2.8.2	Assembly of power modules.....	71
2.8.3	Connecting the module to the power circuit.....	74
2.9	Power assemblies.....	75
2.9.1	Integrated power modules	75
2.9.2	Intellectual power module	75
2.9.3	Power assemblies of basic topology (1/2B2, B2, B6) with a dc element and a cooling system.....	75
2.9.4	Power assemblies of B6U + B6I topology: Inverter platforms.....	76
2.9.5	Power bipolar assemblies	76
2.10	Applications of power switches.....	76
2.11	Cooling systems for semiconductor power devices	77
2.11.1	Radiators for air cooling	78
2.11.2	Radiators for liquid cooling	79
2.12	Promising developments in power electronics	80
2.12.1	Power switches based on SiC.....	80
2.12.2	Highly integrated power modules.....	82
2.13	Control of semiconductor power switches	83
2.14	Passive components.....	86
2.14.1	Introduction.....	86
2.14.2	Electromagnetic components.....	87
2.14.2.1	Basic characteristics of ferromagnetic materials...	87
2.14.2.2	Influence of high frequencies and nonsinusoidal voltage on the operation of transformers and reactors	92
2.14.3	Capacitors: Basic definitions and characteristics	98
2.14.3.1	Influence of the form and frequency of the voltage on capacitor operation	101
	References	105
Chapter 3 Control of power electronic devices.....		107
3.1	Mathematical models.....	107
3.1.1	One-dimensional and multidimensional models.....	107
3.1.2	Linear and nonlinear systems—Linearization	108

3.1.3	Differential and matrix equations—Switching function....	113
3.1.3.1	Equations in terms of deviations.....	117
3.1.3.2	Per-unit equations.....	118
3.1.4	Two-dimensional mathematical description of a three-phase circuit.....	119
3.1.4.1	Motionless Cartesian coordinate system (α, β)....	120
3.1.4.2	Rotating Cartesian coordinate system (d, q).....	121
3.1.4.3	Converting the instantaneous power of a three-phase system to the power of a two-phase system	122
3.1.5	Laplace transformation and transfer function	123
3.1.6	Pulse modulation.....	127
3.1.7	Difference equations	129
3.1.8	Discrete Laplace transformation (Z-transformation)	131
3.2	Analysis of the electrical processes in power electronic devices.....	133
3.2.1	Analytical solution of differential equations.....	133
3.2.1.1	Solution of differential equations by Laplace transformation.....	134
3.2.2	Fitting method.....	135
3.2.3	Phase trajectories and the point-transformation method	136
3.2.4	The primary-component method.....	137
3.2.5	Stability	140
3.3	Control methods	141
3.3.1	Control problems and principles.....	141
3.3.2	Structure of control system	143
3.3.3	Linear control methods.....	145
3.3.3.1	Controller design for one-dimensional control systems.....	145
3.3.3.2	Controller design for multidimensional control systems.....	146
3.3.4	Relay control.....	148
3.3.5	Sliding-mode control.....	151
3.3.5.1	Sufficient conditions for the existence of sliding motion	153
3.3.6	Digital control	156
3.3.7	Predict control	158
3.3.8	Artificial intelligence in power electronics.....	159
3.3.8.1	Fuzzy logic.....	159
3.3.8.2	Neural networks	164
3.3.8.3	Genetic algorithms	168
	Appendix 3A: Newton’s binomial formula	170
	Appendix 3B: Solution of differential equations	171
	References	174

Chapter 4	Line-commutated converters	175
4.1	Introduction.....	175
4.2	Rectifiers.....	176
4.2.1	The rectification principle	176
4.2.1.1	Circuit with active load.....	177
4.2.1.2	Circuit with resistive–inductive load.....	178
4.2.1.3	Counter-emf load.....	179
4.2.2	Basic rectification circuits.....	179
4.2.2.1	Single-phase circuit with center-tapped transformer.....	180
4.2.2.2	Single-phase bridge circuit.....	186
4.2.2.3	Three-phase circuit with center-tapped transformer.....	187
4.2.2.4	Three-phase bridge circuit.....	193
4.2.2.5	Multiple-bridge circuits.....	199
4.2.3	Characteristics of rectifiers.....	202
4.2.3.1	Output voltage ripple.....	202
4.2.3.2	Distortion of the input current.....	203
4.2.3.3	The commutation of the thyristors.....	204
4.2.3.4	External rectifier characteristic.....	207
4.2.3.5	Energy characteristics of rectifiers.....	208
4.3	Grid-tie inverters.....	210
4.3.1	Operating principle.....	210
4.3.1.1	Operation in the inverting mode.....	212
4.3.2	Basic circuits operation in the inverting mode.....	214
4.3.2.1	Single-phase bridge inverter.....	214
4.3.2.2	Three-phase bridge inverter.....	218
4.3.3	Active, reactive, and apparent powers of inverters.....	221
4.3.4	Characteristics of inverters.....	222
4.4	Direct frequency converters (cycloconverters).....	224
4.4.1	Thyristor-based ac–ac converters.....	224
4.4.2	Reducing of the output-voltage distortion.....	228
4.5	ac voltage regulators based on thyristors.....	230
4.5.1	Single-phase ac voltage regulators.....	230
4.5.1.1	Operation with active load.....	233
4.5.1.2	Operation with resistive–inductive load.....	234
4.5.1.3	Operation with inductive load.....	235
4.5.2	Three-phase ac voltage regulators.....	236
	References.....	239
Chapter 5	Conversion from direct current to direct current	241
5.1	Introduction: Continuous stabilizers.....	241
5.2	Basic dc voltage regulators.....	243
5.2.1	Step-down dc/dc converter.....	243